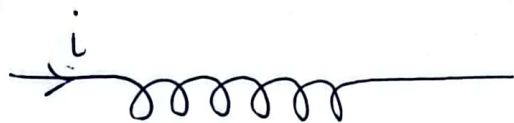


Coefficient of self inductance for a long solenoid



N = total no of turns

n = number of turns per unit length

l = length of solenoid

R = radius of each coil

$$n = \frac{N}{l}$$

B = magnetic field within the solenoid

$$= \mu_0 i n$$

ϕ linked with each coil = $BA = \mu_0 i n \pi R^2$

$$\text{Total flux } \phi_T = N \phi = N \mu_0 n i \pi R^2$$

$$= (nl) \mu_0 n i \pi R^2$$


$$= \mu_0 n^2 \pi R^2 l i$$

$$\Rightarrow L i = \mu_0 n^2 \pi R^2 l i$$


$$\Rightarrow \boxed{L = \mu_0 n^2 \pi R^2 l}$$

Coeff. of self inductance depends on geometry.

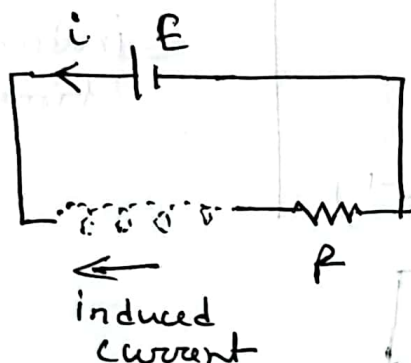At certain time $t = t$ where $0 < t < \infty$, $i = i'$
and $0 < i < i_0$



$\Rightarrow$

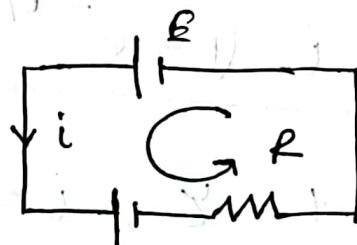

an inductor produces EMF
we can draw a battery

Now, applying Kirchhoff's law:

$$E - L \frac{di}{dt} - iR = 0$$

$$\Rightarrow E - iR = L \frac{di}{dt}$$

$$\Rightarrow \int_0^t \frac{dt}{L} = \int_0^i \frac{di}{E - iR}$$

$$\Rightarrow \frac{t}{L} = -\frac{1}{R} \log_e [E - iR]_0^i$$

$$\Rightarrow -\frac{Rt}{L} = \log_e |E - iR| - \log_e |E|$$

$$\Rightarrow -\frac{Rt}{L} = \log_e \left| \frac{E - iR}{E} \right|$$


$$\Rightarrow -\frac{Rt}{L} = \log_e \left| 1 - \frac{iR}{E} \right|$$

$$\Rightarrow 1 - \frac{iR}{E} = e^{-(R/L)t}$$


$$\Rightarrow \frac{iR}{E} = 1 - e^{-(R/L)t}$$

$$\Rightarrow i = \frac{E}{R} (1 - e^{-(R/L)t})$$


path $\rightarrow$ $\mathcal{E} = +ve$

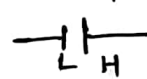


path $\rightarrow$ $\mathcal{E} = -ve$

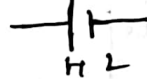

path $\rightarrow$ $-iR$

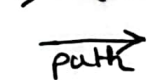

path $\rightarrow$ $+iR$

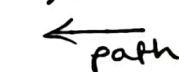

$$\int \frac{dx}{b - ax} = \frac{\log_e |b - ax|}{-a}$$

$$\Rightarrow i = i_0 (1 - e^{-(R/L)t})$$

$$\boxed{i = i_0 (1 - e^{-t/\tau})}$$


$$\tau = \frac{L}{R}$$

= inductive
time const

When, $t = \tau$, $i = i_0 (1 - e^{-1})$


$$\Rightarrow \boxed{i = 0.63 i_0}$$

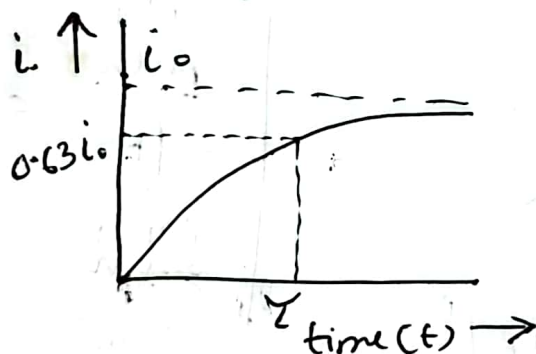τ is that time in which current grows from zero to 63% of its maximum value.



at $t=0$, $i=0$

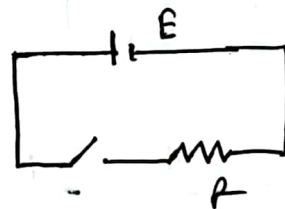No current flows in
branch containing inductor




open circuit
inductor


at $t = \infty$, steady state $i = i_0$

$$i = i_0 (1 - e^{-\infty})$$
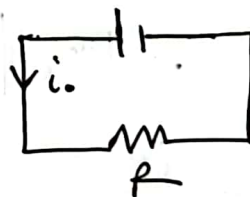
$$= i_0 (1 - \frac{1}{e^{\infty}}) = i_0 (1 - 0) = i_0$$




Short circuit
inductor.

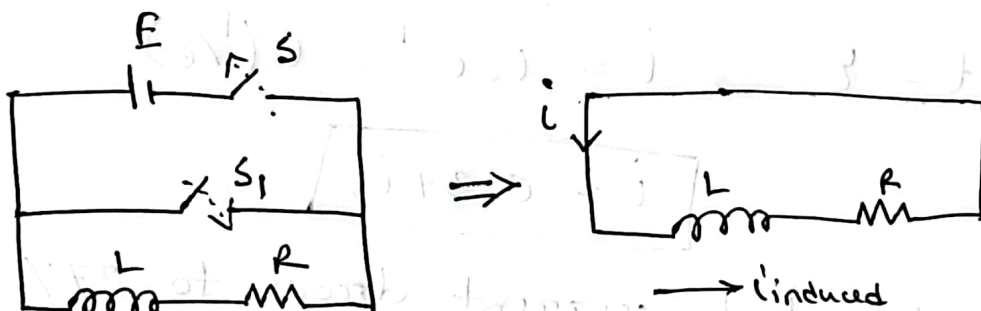

After closing S, current reaches its max value $i_0 = \frac{E}{R}$

Then we open 'S' and close 'S₁'

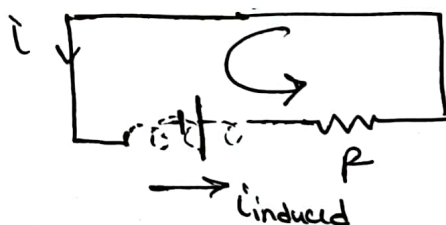- As S is open, battery removed, so the current should be instantly zero, but it will not be the case due to L.
- Inductor will not let current to die as inductor opposes any change.
- Induced current in the same direction.



Apply Kirchhoff's law,

$$-L \frac{di}{dt} - iR = 0$$

$$\Rightarrow -iR = L \frac{di}{dt}$$

$$\Rightarrow -\frac{R}{L} \int_0^t dt = \int_{i_0}^i \frac{di}{i}$$

$$\Rightarrow -\frac{Rt}{L} = \log_e i - \log_e i_0$$

$$\Rightarrow -\frac{Rt}{L} = \log_e \left(\frac{i}{i_0} \right)$$

[as current decreasing so $\frac{di}{dt}$ is -ve]

At $t \rightarrow$
 $i = 0$

$t = 0, i = i_0$

decreasing from max


$$\Rightarrow \frac{i}{i_0} = e^{- (R/L)t}$$

$$\Rightarrow i = i_0 e^{-t/\tau}$$

At, $t = \tau$, $i = i_0 e^{-1} = i_0 (1/e)$

$$i = 0.37 i_0$$

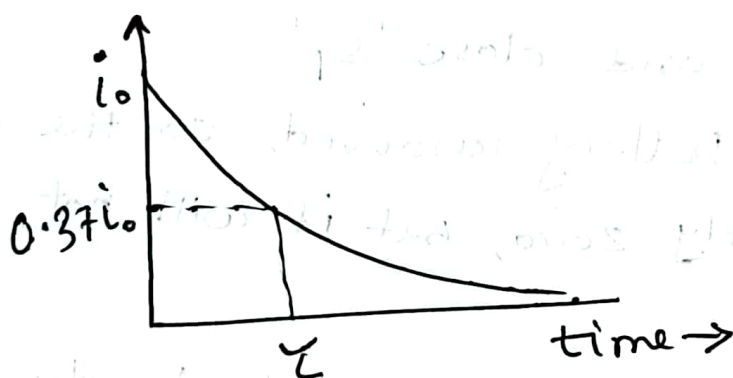Time in which current drops to 37% of initial.



When switch is closed

$$0 = L \frac{di}{dt} + iR$$

$$\frac{di}{dt} + \frac{R}{L} i = 0$$

$$\int \frac{di}{i} = - \int \frac{R}{L} dt$$

$$\ln i = - \frac{R}{L} t + \ln i_0$$