

V-118:-


Multiplexer

→ combinational circuit


↳ that selects binary information from one of many input lines and directs it to o/p line.

Data selector

O/P always 1

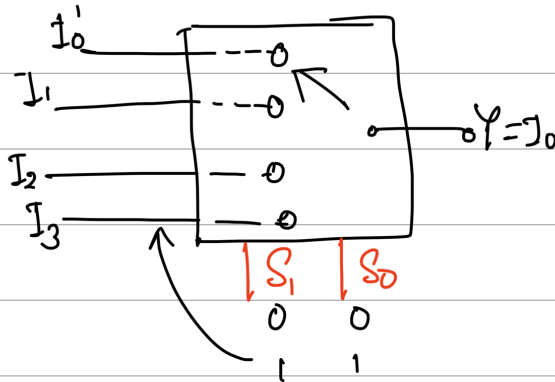

Select line/selector var.

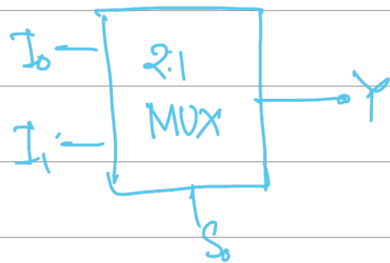

Advantage

1. Reduce no. of wire
2. Reduce circuit complexity
3. Implementation of various circuit using MUX

$n = 2^m$  → no. of select line

no. of I/P


$m = \log_2 n$

$n = 4$   
 $m = 2$

Types:-



2:1, 4:1, 8:1, 16:1, 32:1  
1 2 3 4 5

2:1 MUX:-

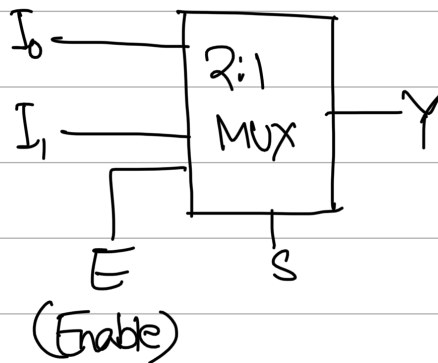

| E | S | Y              |
|---|---|----------------|
| 0 | X | 0              |
| 1 | 0 | I <sub>0</sub> |
| 1 | 1 | I <sub>1</sub> |

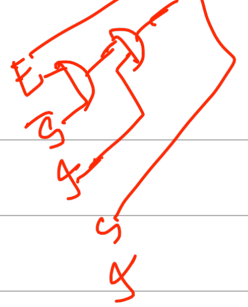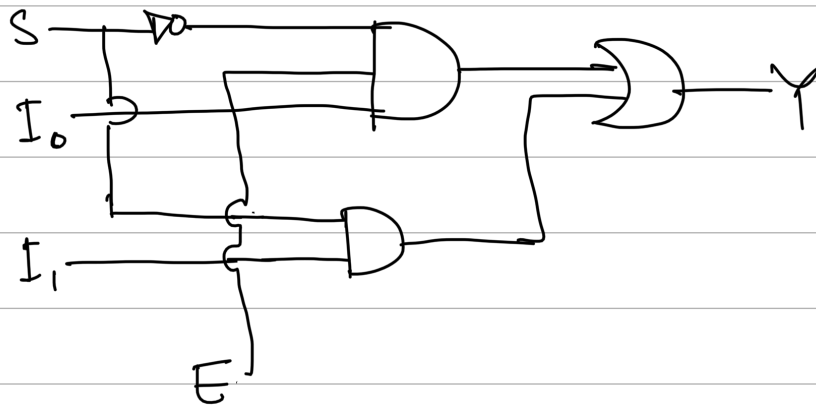
$$Y = E \cdot \bar{S} \cdot I_0 + E \cdot S \cdot I_1$$
  
$$= E (\bar{S} \cdot I_0 + S \cdot I_1)$$



4:1 MUX:-


$$n=4$$

$$m = \log_2 n \\ = \log_2 4 = 2$$

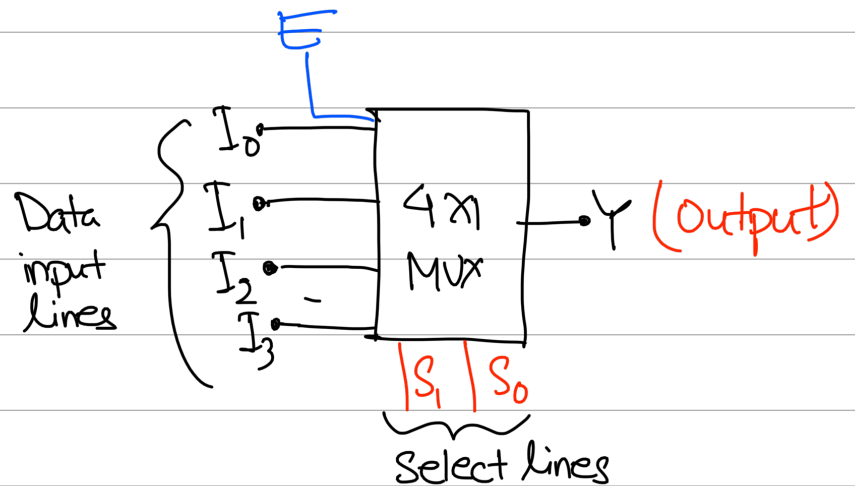

| $S_1$ | $S_0$ | $Y$   |
|-------|-------|-------|
| 0     | 0     | $I_0$ |
| 0     | 1     | $I_1$ |
| 1     | 0     | $I_2$ |
| 1     | 1     | $I_3$ |
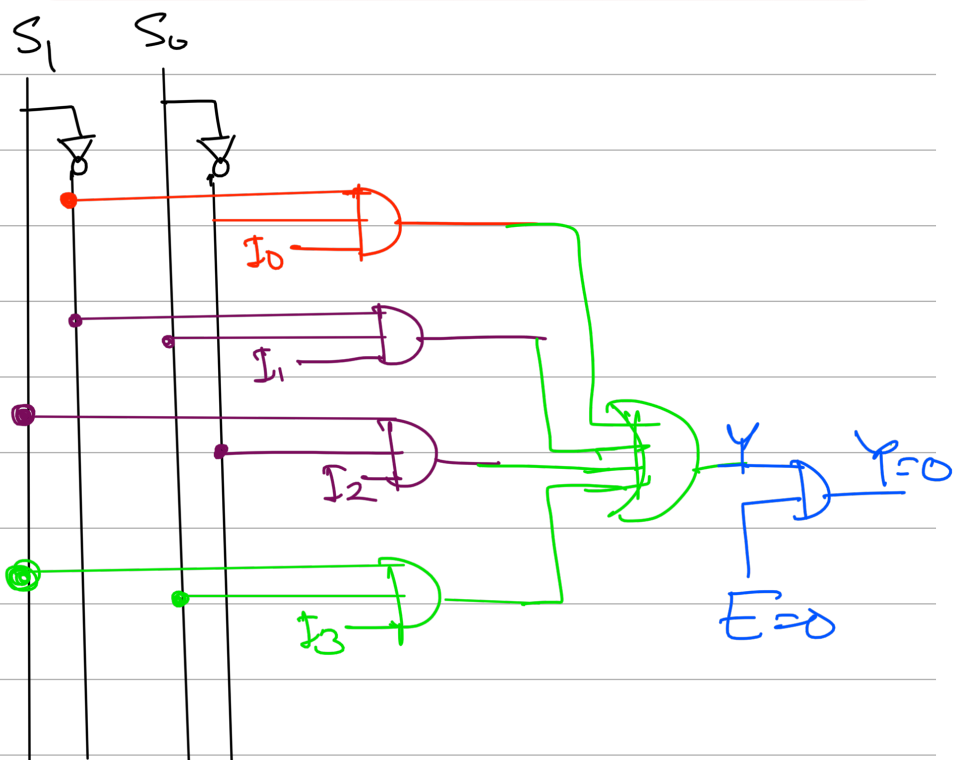
$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$




# 8x1 MUX:-


$$n=8$$

$$m = \log_2 8 = 3$$

| $S_2$ | $S_1$ | $S_0$ | $Y$   |
|-------|-------|-------|-------|
| 0     | 0     | 0     | $I_0$ |
| 0     | 0     | 1     | $I_1$ |
| 0     | 1     | 0     | $I_2$ |
| 0     | 1     | 1     | $I_3$ |
| 1     | 0     | 0     | $I_4$ |
| 1     | 0     | 1     | $I_5$ |
| 1     | 1     | 0     | $I_6$ |
| 1     | 1     | 1     | $I_7$ |

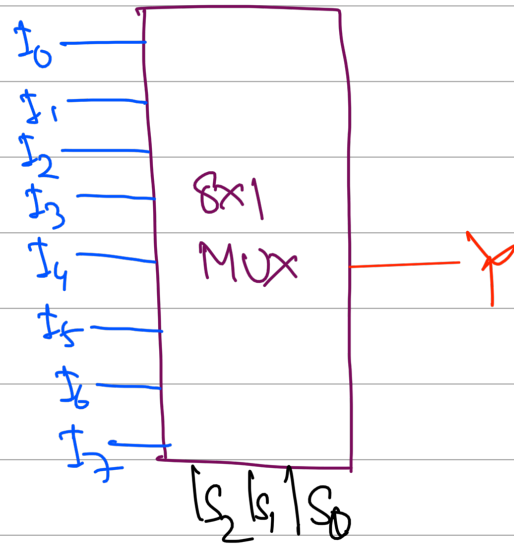

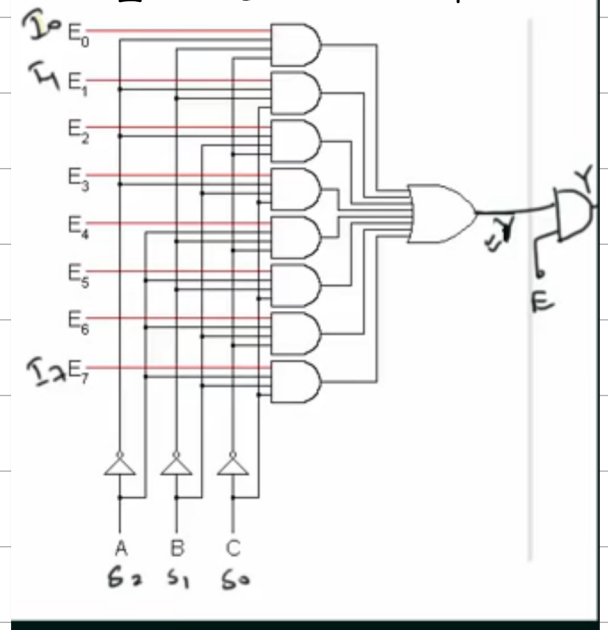
$$Y = \overline{S_2} \overline{S_1} \overline{S_0} I_0 + \overline{S_2} \overline{S_1} S_0 I_1 + \overline{S_2} S_1 \overline{S_0} I_2 + \overline{S_2} S_1 S_0 I_3 + S_2 \overline{S_1} \overline{S_0} I_4 + S_2 \overline{S_1} S_0 I_5 + S_2 S_1 \overline{S_0} I_6 + S_2 S_1 S_0 I_7$$


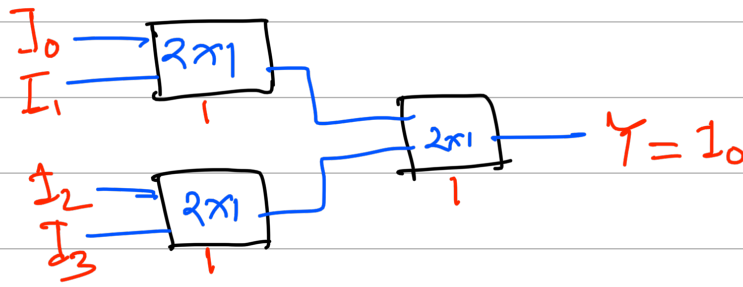
## # MUX tree Basic / 4x1 MUX using 2x1 MUX

$$\frac{4}{2} = 2$$

$$\frac{2}{1} = 1 \quad + \quad (3) \rightarrow 2 \times 1 \text{ MUX}$$



| $-S_1$ | $S_0$ | $Y$   |
|--------|-------|-------|
| 0      | 0     | $I_0$ |
| 0      | 1     | $I_1$ |
| 1      | 0     | $I_2$ |
| 1      | 1     | $I_3$ |

Q) 8x1 MUX by 2x1 :-

| $S_2$ | $S_1$ | $S_0$ | $Y$   |
|-------|-------|-------|-------|
| 0     | 0     | 0     | $I_0$ |
| 0     | 0     | 1     | $I_1$ |
| 0     | 1     | 0     | $I_2$ |
| 0     | 1     | 1     | $I_3$ |
| 1     | 0     | 0     | $I_4$ |
| 1     | 0     | 1     | $I_5$ |
| 1     | 1     | 0     | $I_6$ |
| 1     | 1     | 1     | $I_7$ |

$$n_1 = 8$$


$$n_2 = 2$$

$$\frac{8}{2} = 4$$

$$\frac{4}{2} = 2$$

$$\frac{2}{2} = 1$$

$= 7$

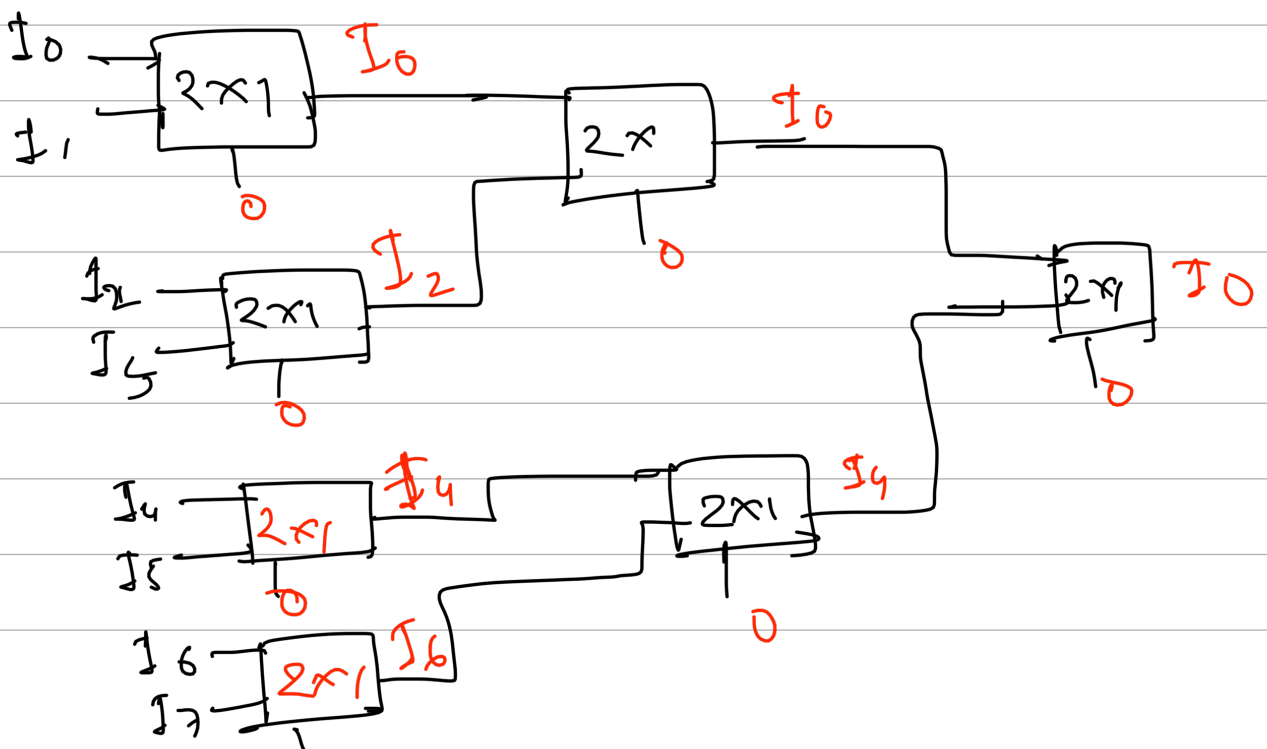




# 8X1MUX USING 4X1 (SP) :


8X

| $S_2$ | $S_1$ | $S_0$ | $Y$   |
|-------|-------|-------|-------|
| 0     | 0     | 0     | $I_0$ |
| 0     | 0     | 1     | $I_1$ |
| 0     | 1     | 0     | $I_2$ |
| 0     | 1     | 1     | $I_3$ |
| 1     | 0     | 0     | $I_4$ |
| 1     | 0     | 1     | $I_5$ |
| 1     | 1     | 0     | $I_6$ |
| 1     | 1     | 1     | $I_7$ |

using enable can imp.

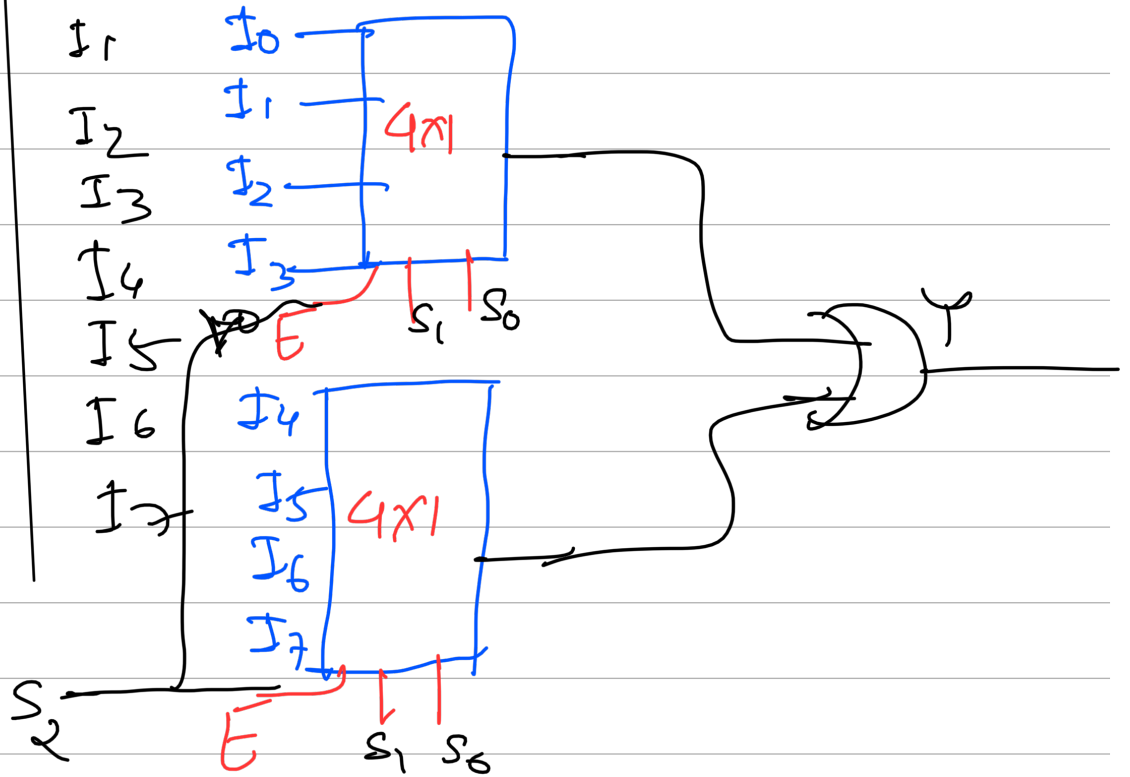

## 32X1 USING 8X1

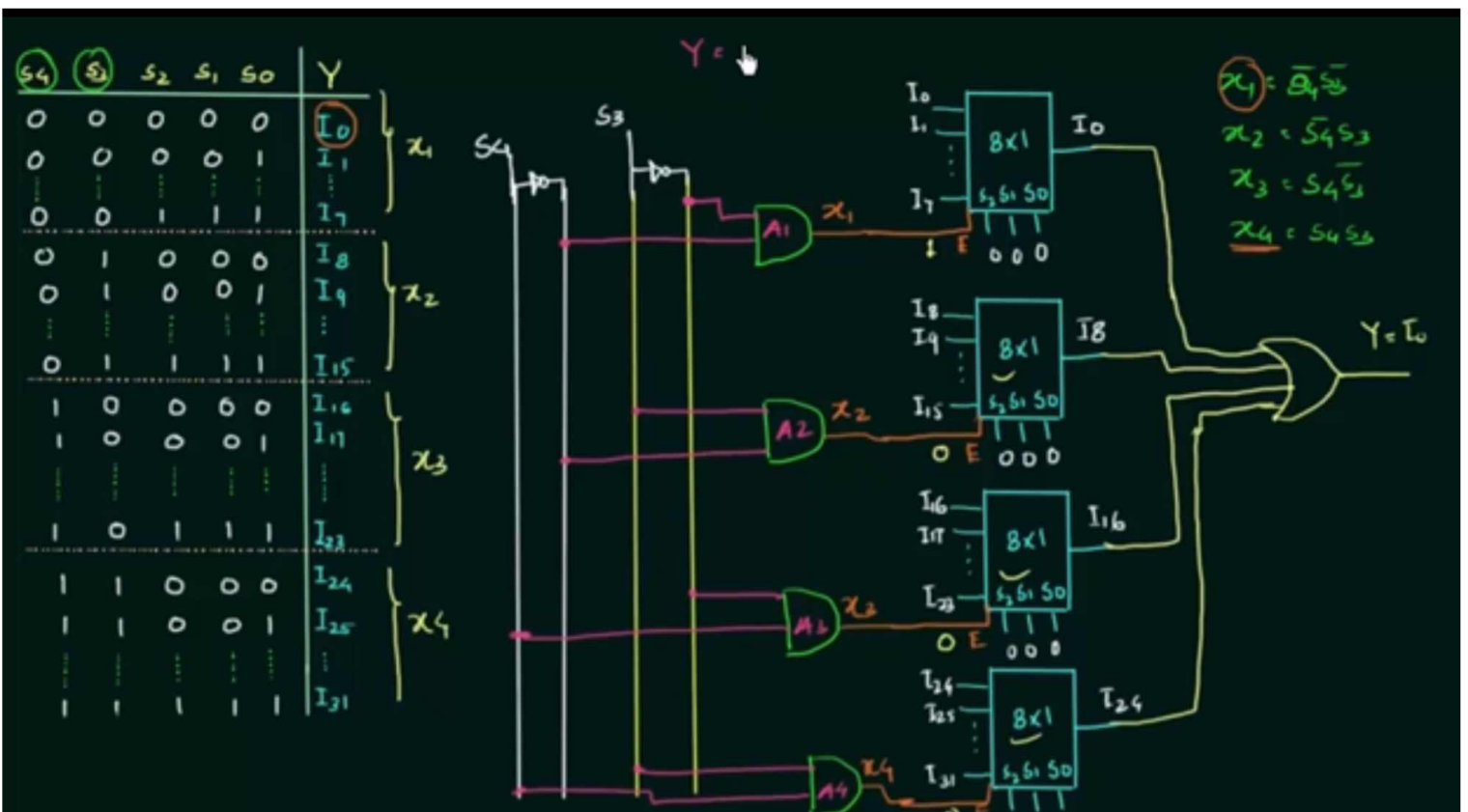

# # Implementation of Boolean Function using MUX

Implement:-  $F(A, B, C, D) = \sum m(1, 4, 5, 7, 9, 12, 13)$  using MUX(4x1)

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      |    | 1  |    |    |
| 01      | 1  | 1  | 1  |    |
| 11      |    | 1  | 1  |    |
| 10      |    | 1  |    | 1  |


| A | B | S <sub>1</sub> | S <sub>0</sub> | Y                   |
|---|---|----------------|----------------|---------------------|
| 0 | 0 | 0              | 0              | $S_0 = \bar{C}D$    |
| 0 | 1 | 0              | 1              | $I_1 = D + \bar{C}$ |
| 1 | 0 | 1              | 0              | $I_2 = \bar{C}D$    |
| 1 | 1 | 1              | 1              | $I_3 = \bar{C}$     |

$$\bar{C}D = I_0$$

$$\bar{C} + D = I_1$$

$$\bar{C} = I_3$$

$$\bar{C}D = I_2$$

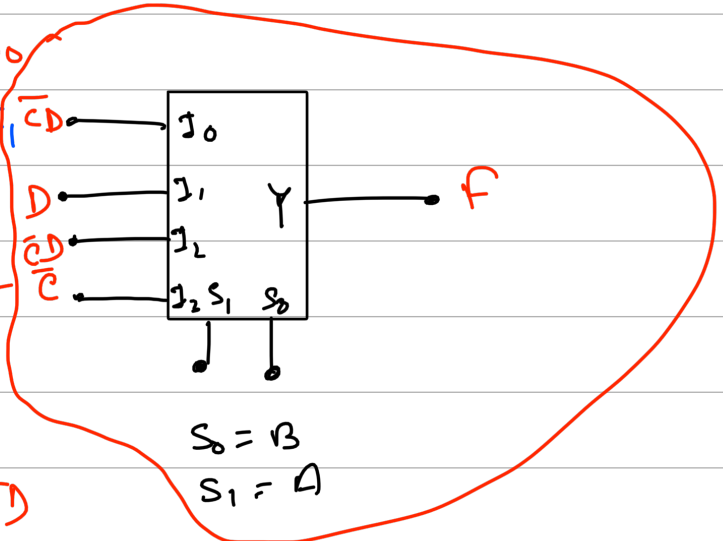

## # 1 bit FA using 4x1 MUX :-


| A | B | C <sub>in</sub> | S | C <sub>o</sub> |
|---|---|-----------------|---|----------------|
| 0 | 0 | 0               | 0 | 0              |
| 0 | 0 | 1               | 1 | 0              |
| 0 | 1 | 0               | 1 | 0              |
| 0 | 1 | 1               | 0 | 1              |
| 1 | 0 | 0               | 1 | 0              |
| 1 | 0 | 1               | 0 | 1              |
| 1 | 1 | 0               | 0 | 1              |
| 1 | 1 | 1               | 1 | 1              |

for S

| A \ B C <sub>i</sub> | 00 | 01 | 11 | 10 |
|----------------------|----|----|----|----|
| 0                    | 1  | 1  |    | 1  |
| 1                    | 1  |    | 1  |    |

for C<sub>o</sub>

| A \ B C <sub>i</sub> | 00 | 01 | 11 | 10 |
|----------------------|----|----|----|----|
| 0                    |    |    |    |    |
| 1                    |    |    |    |    |

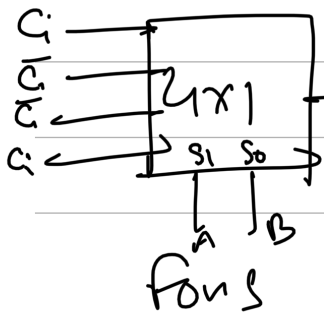

| A | B | S                 |
|---|---|-------------------|
| 0 | 0 | $I_0 = C_0$       |
| 0 | 1 | $I_1 = \bar{C}_i$ |
| 1 | 0 | $I_2 = \bar{C}_i$ |
| 1 | 1 | $I_3 = C_i$       |

